



Fluid Power Technology
NVQ Level 5 Semester I Examination

Applied Electrical and Electronics – E40C00M04

Instructions to Candidates:

1. Answer five (05) questions

Total Time: 03 hours

Total Marks: 100

Q1.

- State the ohm's law.
- From the Figure 1 find,

(01 Mark)

(06 Marks)

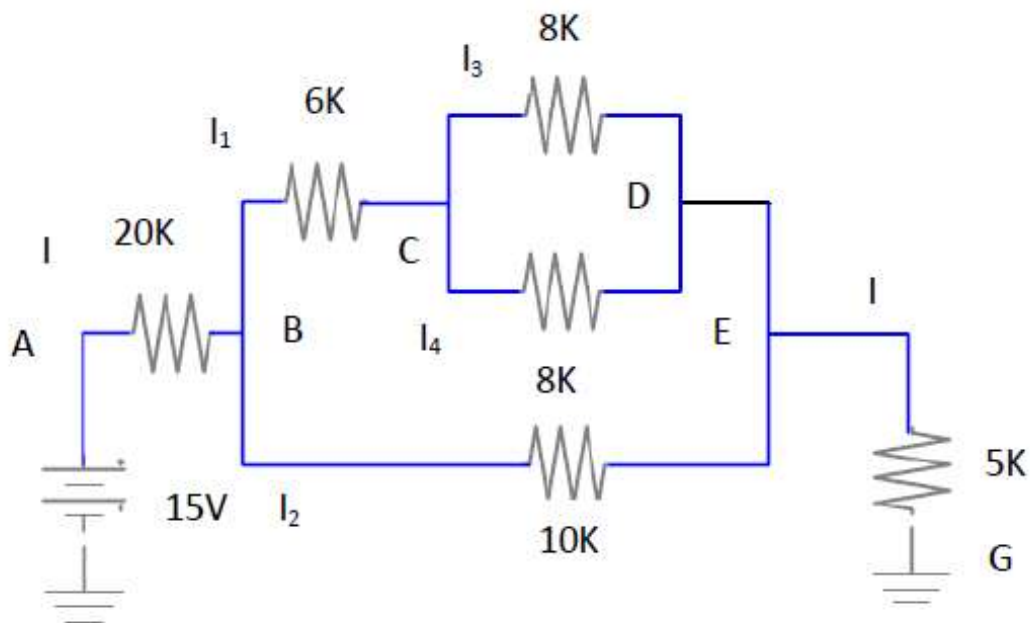


Figure 1

- Resistance of the entire circuit.
- Current in each resistor.
- Voltage drops across 10K resistor.

c. Find the voltage V_{AB} in the circuit shown Figure2.

(03 Marks)

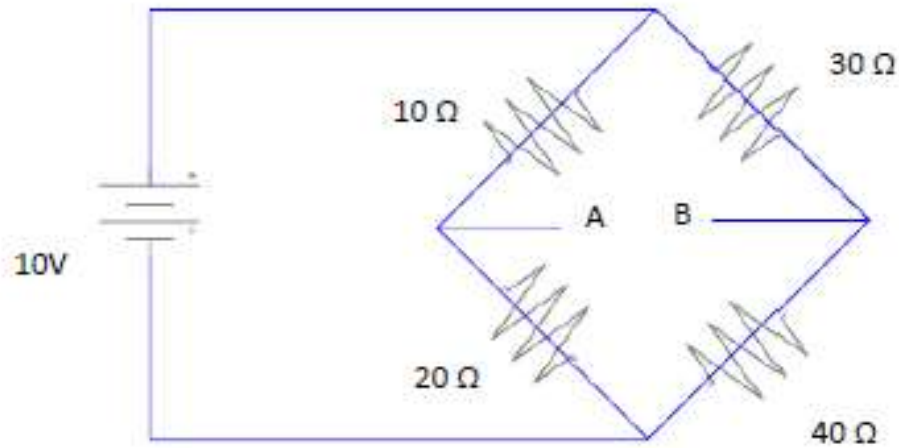


Figure 2

d.


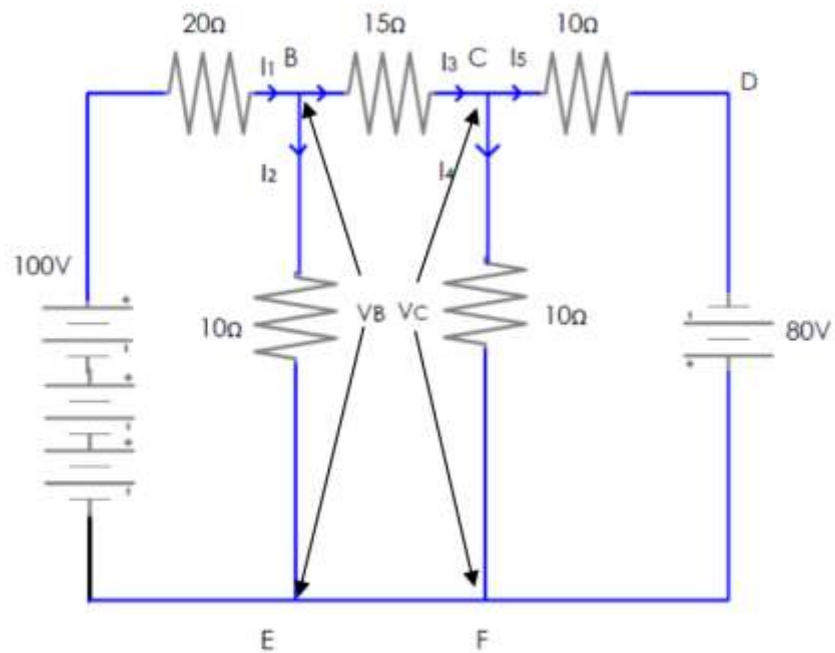


Figure 3

Find the currents in the various branches of the circuit in Figure 3 by nodal analysis. (10 Marks)

Q2

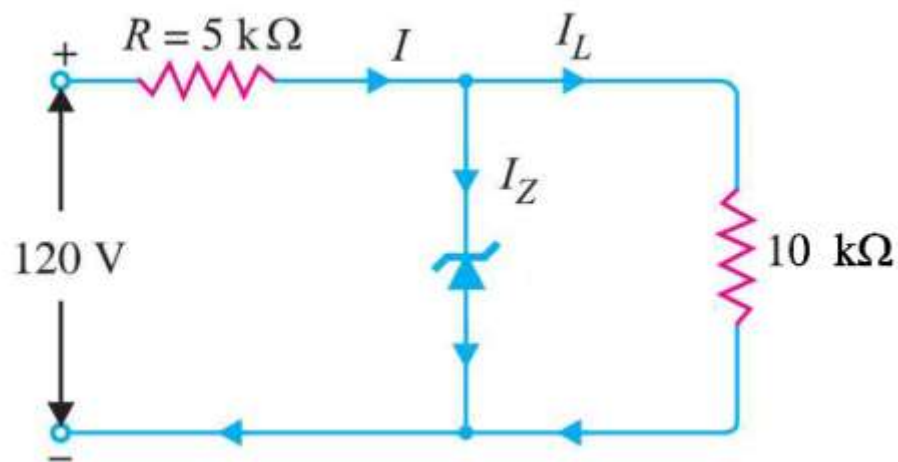- a) Draw the VI characteristics of Zener diode and show the main regions (05 Marks)
- b) Zener diode finds numerous applications in transistor circuitry. what are common uses (03 Marks)
- c) Using the Zener Diode circuit shown in figure 2, compute the following.
Consider Zener Voltage (V_Z) = 50V
- State weather the Zener diode is in “On Stage” or “Off Stage”
 - Voltage across the 10 k Ω
 - Voltage drop through the series resister (R)
 - Current through the diode (I_Z)
- (12 Marks)



Q3

- a) Draw the input characteristic curve for common emitter transistor. (4 Marks)
- b) In the collection- feedback bias circuit $V_{cc} = 12\text{V}$ of figure 2 compute (16 Marks)
- The three transistor currents.
 - Drop across R_c and R_B
 - Value of V_{CE}

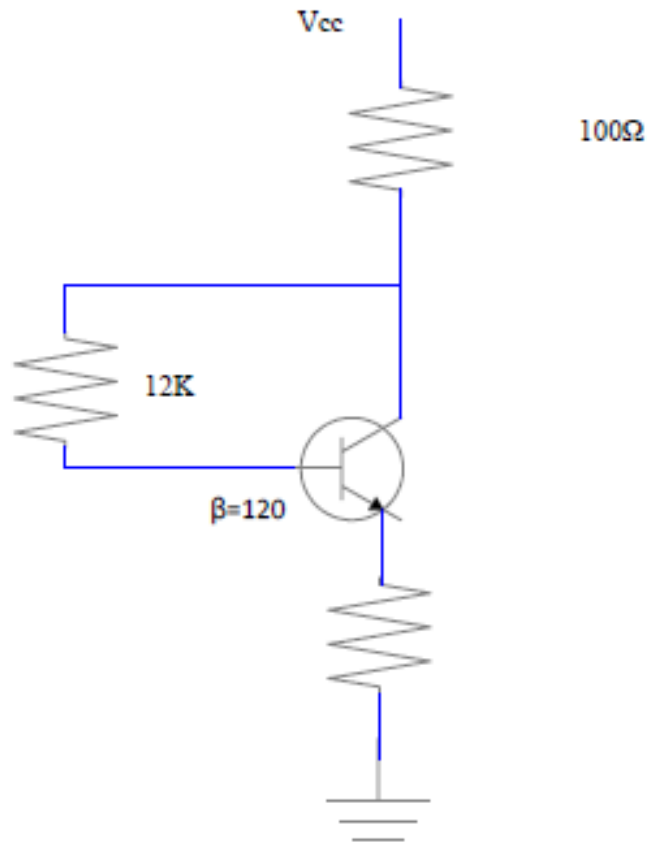


Figure 2

Q4

a. Draw logic circuit solutions for the below Boolean expression.

(08 Marks)

i. $(A + B) \cdot \overline{C} \cdot (D + E) = Y.$

ii. $\overline{A} \cdot (B + C) \cdot D = Y.$

iii. $A + (B \cdot C) + \overline{D} = Y.$

iv. $A \cdot B + \overline{C} + D \cdot E = Y.$


b. Simplify the Boolean expression from Karnaugh maps (K Maps)

(12 Marks)

a) $A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + AB\bar{C} = Y$

b) $A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}BCD + A\bar{B}\bar{C}D = Y$

Q5

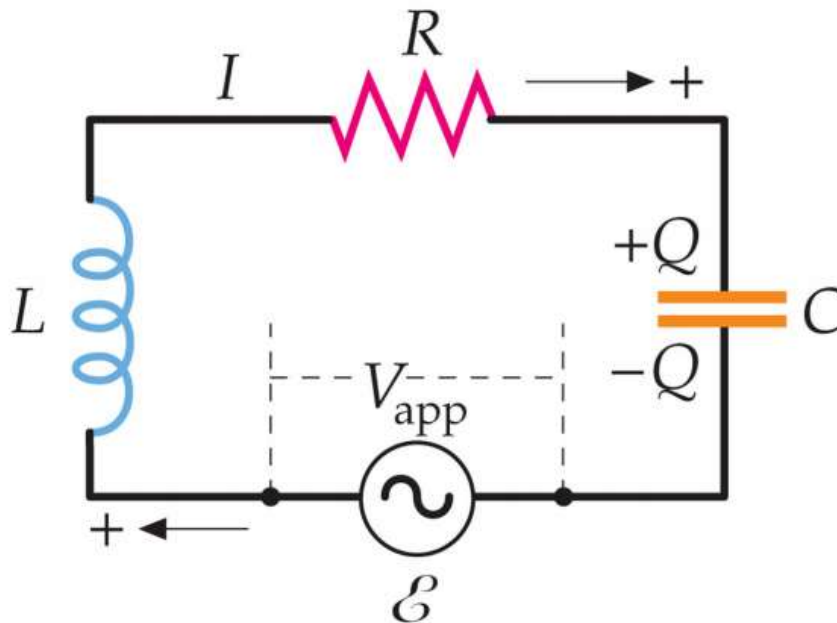

$R = 250\ \Omega$, $L = 1.20\text{mH}$, $C = 1.80\ \mu\text{F}$, $V_p = 120\text{v}$, $f = 60\text{Hz}$ Determine the following:

- (a.) X_L - Inductive reactance
- (b.) X_C - Capacitive reactance
- (c.) Z - Impedance
- (d.) θ - Phase angle
- (e.) I_p - Peak current

(20 Marks)